## Expressões booleanas obtidas de tabela-verdade

## Tabelas

A	В	s
0	0	1
0	1	0
1	0	1
1	1	1

Α	В	С	S
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Α	В	С	D	S
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0 0 0	1 1	0	1	0 0 0 1 0 1 0 1 0 0
0	1		0	1
0	1	1	1	0
0 1 1 1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0 0
1	1	1	1	0

## Obrigado!!